



Finite State Machine

Bynaboyina Aiswarya
Roll No: FWC22295
aiswaryabaiswarya61@gmail.com

I. ABSTRACT

This paper explains a Finite State Machine by deconstructing the decade counter and here we verified the both incrementing decoder from 0 to 9 and decrementing decoder from 9 to 0 using arduino uno.

II. COMPONENTS

The required components list is given in Table: I., seven segment display is shown in Fig.1, and 7474 D-Flip Flop pin diagram is shown in Fig-2.

Components	Value	Quantity
IC	7474	2
seven segment display		1
Arduino	UNO	1
Jumper Wires		50
Breadboard		1

TABLE I

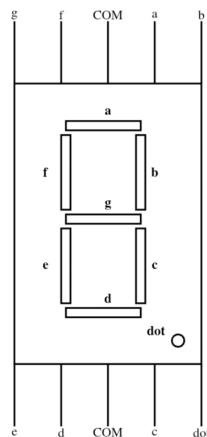


Fig. 1.

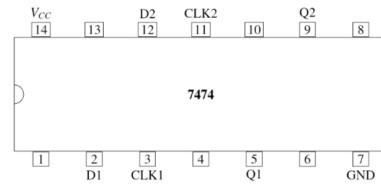


Fig. 2.

III. PROCEDURE

- 1) Make the connections of arduino, and two 7474 ICs according to Fig-4.

	INPUT				OUTPUT				CLOCK		5V			
	W	X	Y	Z	A	B	C	D						
Arduino	D6	D7	D8	D9	D2	D3	D4	D5	D13					
7474	5	9			2	12			CLK1	CLK2	1	4	10	13
7474			5	9			2	12	CLK1	CLK2	1	4	10	13
7447					7	1	2	6			16			

Fig. 3.

- 2) Block diagram of fsm for decade counter

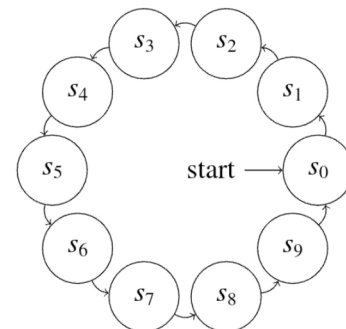


Fig. 4.

3) Block diagram of Decade Counter.

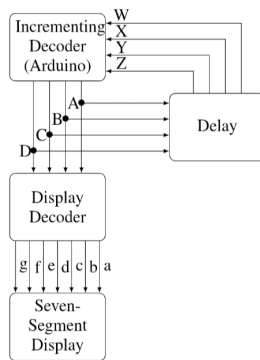


Fig. 5.

4) Block diagram of Decade Counter FSM implementation using D-Flip Flops.

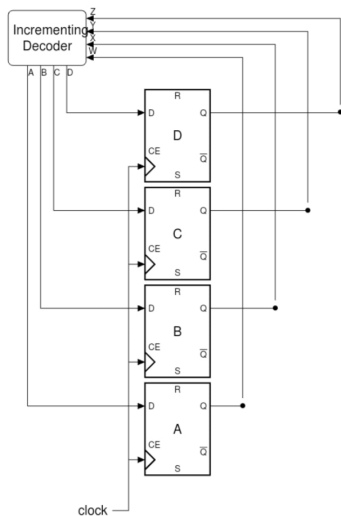


Fig. 6.

5) Truth Table for incrementing from 0 to 9 in seven segment display

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE II

6) Truth Table for decrementing from 9 to 0 in seven segment display

Z	Y	X	W	D	C	B	A
0	0	0	0	1	0	0	1
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	1
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	1
0	1	1	1	0	1	1	0
1	0	0	0	0	1	1	1
1	0	0	1	1	0	0	0

TABLE III

7) Execute the arduino code without any errors.

8) After upload the code into hardware setup using arduino IDE platform with hex file.

IV. RESULTS

1) Download the code given in the link below and execute them to see the output as shown in Fig.6,7.

2) Increment - https://github.com/BynaboyinaAiswarya/Fwc-/blob/main/Ide/FSM/txt_inc.cpp

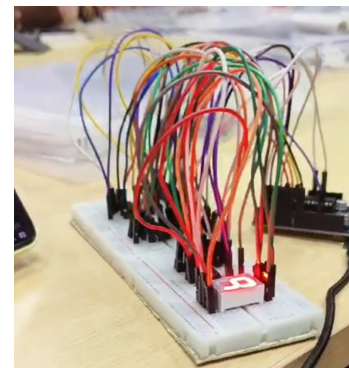


Fig. 7.

3) Decrement - https://github.com/BynaboyinaAiswarya/Fwc-/blob/main/Ide/FSM/txt_dec.cpp

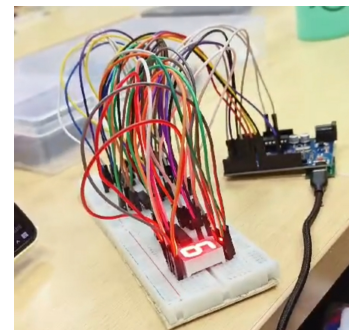


Fig. 8.

V. CONCLUSION

Hence implementation of 7474 IC Decade Counter on Seven segment display using arduino UNO is done.